



ELECTRICAL ENGINEERING

DC Circuit

Hand Notes For GATE, IES, PSUs etc...

Hand Notes


Page Length : 36

Note : We also providing IIT JEE, Advance, NEET, JEE UG, GATE, IES, PSUs & Competitive Exam Materials [Handnotes, Shortnotes & Books], All Reports [Seminar Reports & PPT]

Goto : www.martcost.com

Covered Topics :

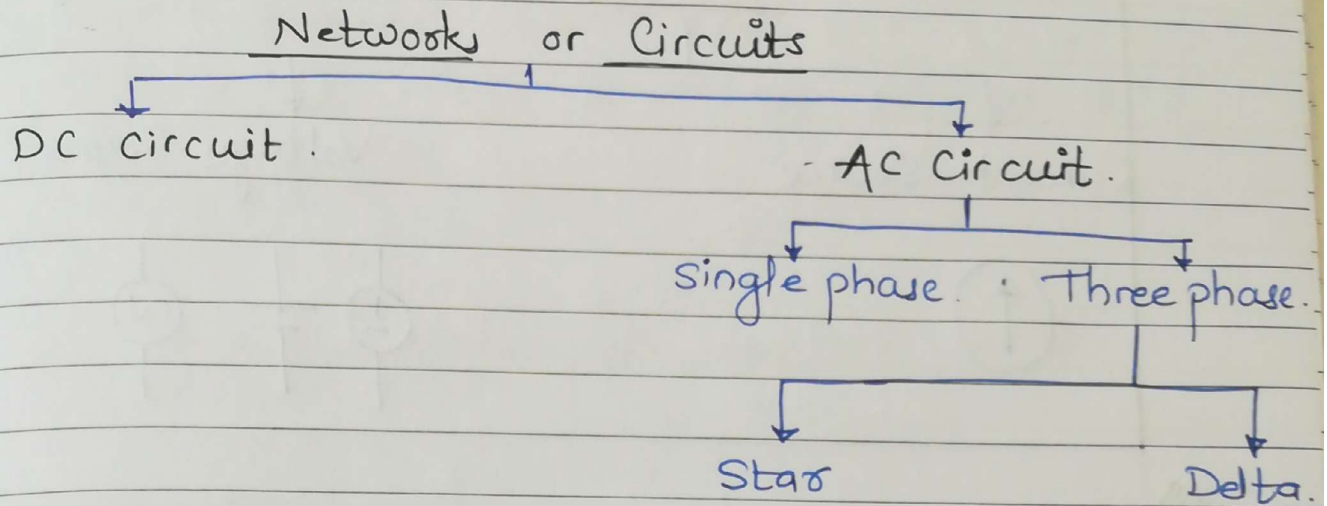- Network of Circuits
- Classification
- DC Circuits
- Series & Parallel Connections
- Voltage Division Rule
- Source Transformation
- Laws
- Star to Delta Transformation
- Node Analysis
- Mesh Analysis
- Superposition Theorem
- Thevenins Theorem
- Norton's Theorem



Electrical Circuits & Networks :-

• Network or Circuit \Rightarrow

A network or circuit is an electrical arrangement in which circuit elements (R, L & C) & sources (voltage & current source).

• Circuit Elements \Rightarrow

(Energy Waste)

1) Resistor



(R)

unit: Ω

$$R = \rho \cdot \frac{l}{a}$$

$$R = \frac{V}{I}$$

(Energy stored in Magnetic field)

2) Inductor




(L)

Henry (H)

$$L = \frac{N\Phi}{I}$$

(Energy stored in Electrical field)

3) Capacitor

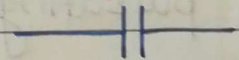


(C)

Farade (F)

$$C = \epsilon \frac{A}{d}$$

$$C = \frac{Q}{V}$$

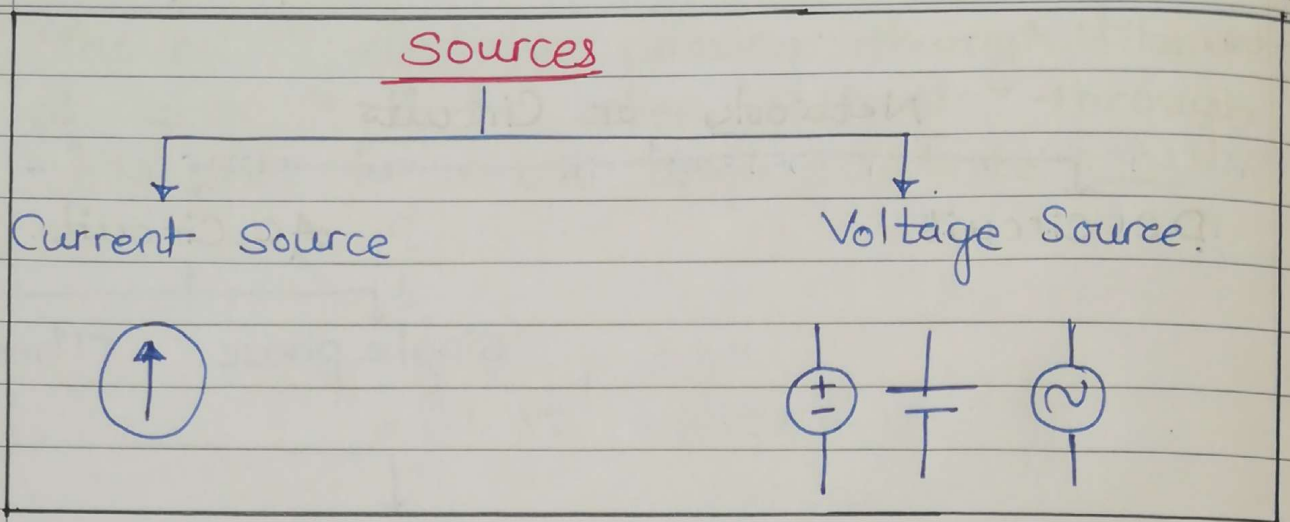

Depending upon Source

classification of Network or Circuits.

